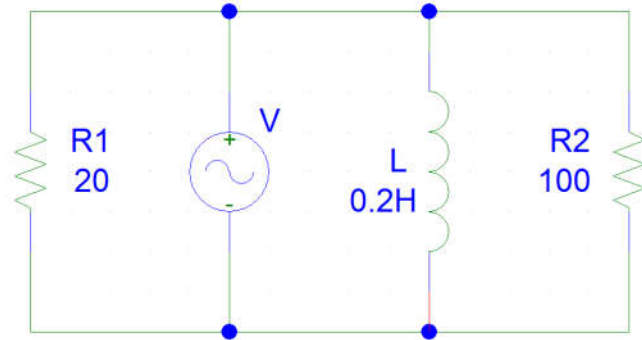


$$R_1 := 20 \Omega \quad R_2 := 100 \Omega$$

$$L := 0.2 \text{ H}$$

$$V := (5 \angle 180^\circ) \text{ V} \quad \omega := 1000 \frac{\text{rad}}{\text{s}}$$

$$X_L := j \cdot \omega \cdot L = 200i \Omega$$



Calcolare la corrente sul generatore
Verificare che la corrente sul generatore è pari alla somma delle correnti su R1, R2 ed L

$$Z_1 := \frac{R_2 \cdot X_L}{R_2 + X_L} = \frac{100 \cdot j 1000 \cdot 0.2}{100 + j 1000 \cdot 0.2} = \frac{j 20000}{100 + j 200} = \frac{j 200}{1 + j 2} \cdot \frac{1 - j 2}{1 - j 2}$$

$$= \frac{j 200 + 400}{1 - 4} = \frac{400}{5} - j \frac{200}{5} = 80 - j 40 \Omega \quad Z_1 = (80 + 40i) \Omega$$

$$= \sqrt{80^2 + 40^2} \angle \text{atg} \left(\frac{40}{80} \right) = 89.443 \Omega \angle 26.565$$

$$\text{polar}(Z_1) = [89.443 \Omega \quad 26.565]$$

$$Z_{\text{tot}} := \frac{R_1 \cdot Z_1}{R_1 + Z_1}$$

$$= \frac{20 \cdot 89.443 \angle 26.565}{20 + 80 + j 40} = \frac{1.789 \cdot 10^3 \angle 26.565}{100 + j 40} = \frac{1.789 \cdot 10^3 \angle 26.565}{\sqrt{100^2 + 40^2} \angle \text{atg} \left(\frac{40}{100} \right)}$$

$$= \frac{1.789 \cdot 10^3 \angle 26.565}{107.703 \angle \text{atg} \left(\frac{40}{100} \right)} = \frac{1.789 \cdot 10^3}{107.703} \angle (26.565 - 75.964) = 16.609 \Omega \angle (4.764)$$

$$\text{polar}(Z_{\text{tot}}) = [16.609 \Omega \quad 4.764]$$

$$= 16.609 \cdot \cos(4.764) + j 16.609 \cdot \sin(4.764) = 16.552 + j \cdot 1.379 \Omega$$

$$Z_{\text{tot}} = (16.552 + 1.379i) \Omega$$

$$I := \frac{V}{Z_{\text{tot}}} = \frac{5 \angle 180}{16.609 \angle 4.764} = \frac{5}{16.609} \angle (180 - 4.764) = 0.301 \text{ A} \angle (175.236)$$

$$\text{polar}(I) = [(301.04 \cdot 10^{-3}) \text{ A} \quad 175.236]$$

$$= 0.301 \cdot \cos(175.236) + j 0.301 \cdot \sin(175.236) = -0.3 + j \cdot 0.025 \text{ A}$$

$$I = (-300 \cdot 10^{-3} + 25i \cdot 10^{-3}) \text{ A}$$

In alternativa e molto più velocemente:

$$Y := \frac{1}{Z_{\text{tot}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{j \omega L} = \frac{1}{20} + \frac{1}{100} + \frac{1}{j 200} = 0.05 + 0.01 - j \cdot 0.005$$

$$= 0.06 - j \cdot 0.005 = \sqrt{0.06^2 + 0.005^2} \angle \text{atg} \left(\frac{-0.005}{0.06} \right) = 60.208 \cdot 10^{-3} \angle -4.764$$

$$I := V \cdot Y = (5 \angle 180^\circ) \cdot (60.208 \cdot 10^{-3} \angle -4.764^\circ) = 0.301 \text{ A} \angle (175.236)$$

Calcolo delle correnti sui 3 componenti passivi:

$$I_{R1} := \frac{V}{R_1} = \frac{5 \angle 180}{20} = 0.25 \text{ A} \angle 180^\circ = -0.25 \text{ A} \quad I_{R1} = (-250 \cdot 10^{-3} + 30.615i \cdot 10^{-18}) \text{ A}$$

$$\text{polar}(I_{R1}) = [(250 \cdot 10^{-3}) \text{ A } 180]$$

$$I_{R2} := \frac{V}{R_2} = \frac{5 \angle 180}{100} = 0.05 \text{ A} \angle 180^\circ = -0.05 \text{ A} \quad I_{R2} = (-50 \cdot 10^{-3} + 6.123i \cdot 10^{-18}) \text{ A}$$

$$\text{polar}(I_{R2}) = [(50 \cdot 10^{-3}) \text{ A } 180]$$

$$I_L := \frac{V}{X_L} = \frac{5 \angle 180}{j \cdot 200} = \frac{5 \angle 180}{200 \angle 90} = 0.025 \text{ A} \angle 90^\circ = j \cdot 0.025 \text{ A}$$

$$I_L = (3.062 \cdot 10^{-18} + 25i \cdot 10^{-3}) \text{ A}$$

$$\text{polar}(I_L) = [(25 \cdot 10^{-3}) \text{ A } 90]$$

Verifica che la somma delle 3 correnti calcolate sia pari ad I sul generatore

$$I_{R1} + I_{R2} + I_L = -0.25 - 0.05 + j \cdot 0.025 = -0.30 + j \cdot 0.025 \text{ A} = I$$

$$I_{R1} + I_{R2} + I_L = (-300 \cdot 10^{-3} + 25i \cdot 10^{-3}) \text{ A}$$