

DEFINIZIONE FUNZIONI

$$j := 1i \quad fase(x) := \text{angle}(\text{Re}(x), \text{Im}(x)) \quad eff(x) := \frac{|x|}{\sqrt{2}}$$

DATI

$$\omega := 2.5 \cdot 10^9 \frac{\text{rad}}{\text{s}} \quad T := \frac{2 \cdot \pi}{\omega} = 2.513 \text{ ns} \quad V := 6 \text{ V} \angle 65^\circ$$

$$R := 1.5 \text{ k}\Omega \quad V_M := |V| = 6 \text{ V} \quad \alpha_v := fase(V) = 65^\circ$$

$$L := 0.42 \text{ }\mu\text{H} \quad V = (2.536 + 5.438i) \text{ V}$$

CALCOLO Z e i(t)

$$v(t) := V_M \sin(\omega \cdot t + \alpha_v)$$


$$Z_s := R + j \cdot \omega \cdot L = (1.5 \cdot 10^3 + 1.05i \cdot 10^3) \Omega \quad |Z_s| = (1.831 \cdot 10^3) \Omega$$

$$\varphi := fase(Z_s) = 34.992^\circ$$

$$I := \frac{V}{Z_s} = (0.003 + 0.002i) \text{ A} \quad I_M := |I| = 3.277 \text{ mA} \quad \alpha_i := fase(I) = 30.008 \text{ deg}$$

$$i(t) := I_M \sin(\omega \cdot t + \alpha_i)$$

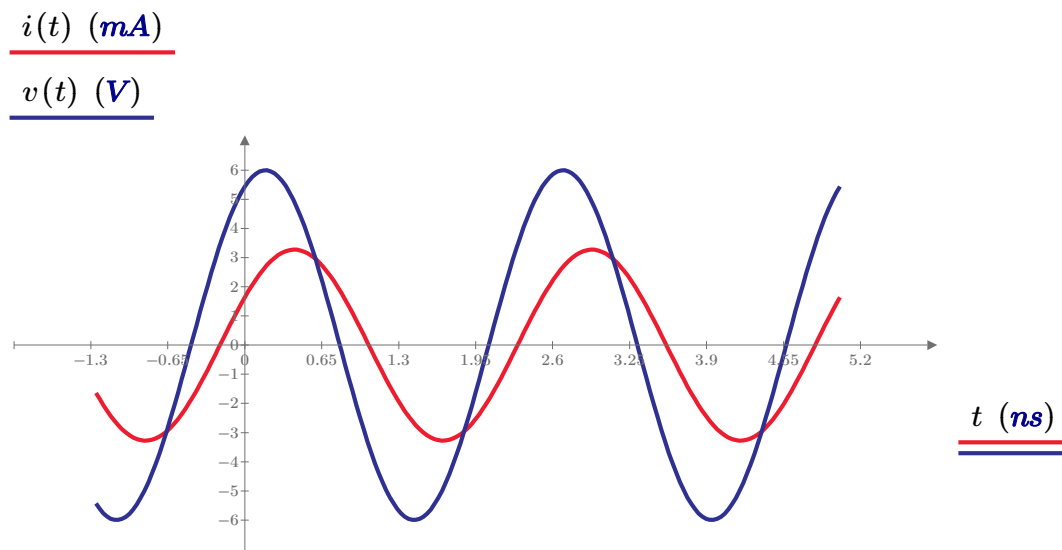GRAFICI CORRENTE E TENSIONE (prima del rifasamento)



CAPACITA' DI RIFASAMENTO

$$C := \frac{L}{|Z_s|^2} = (1.253 \cdot 10^{-13}) \text{ F} \quad X_c := \frac{1}{j \cdot \omega \cdot C} = -3.193i \cdot 10^3 \text{ } \Omega$$

$$Z_p := \frac{Z_s \cdot X_c}{Z_s + X_c} = (2.235 \cdot 10^3 + 2.042i \cdot 10^{-13}) \text{ } \Omega \quad \text{fase}(Z_p) = 9.136 \cdot 10^{-17}$$

la fase di Z_p è piccolissima ($\cong 0$)

POTENZA

$$V_E := \text{eff}(V) = 4.243 \text{ V}$$

$$I_E := \text{eff}(I) = 0.002 \text{ A}$$

$$P_{ist}(t) := V_E \cdot I_E \cdot \cos(\varphi) - V_E \cdot I_E \cdot \cos(2 \omega \cdot t + \alpha_v + \alpha_i) \quad \text{POTENZA ISTANTANEA}$$

$$P_{flut}(t) := -V_E \cdot I_E \cos(2 \cdot \omega \cdot t + \alpha_v + \alpha_i) \quad \text{POTENZA FLUTTUANTE}$$

$$P := V_E \cdot I_E \cdot \cos(\varphi) = 8.054 \text{ mW} \quad \text{POTENZA ATTIVA}$$

$$Q := V_E \cdot I_E \cdot \sin(\varphi) = 5.638 \text{ mW} \quad [\text{VAR}] \quad \text{POTENZA REATTIVA}$$


GRAFICI POTENZE

Q (mW)

$P_{flut}(t)$ (mW)

$P_{ist}(t)$ (mW)

P (mW)

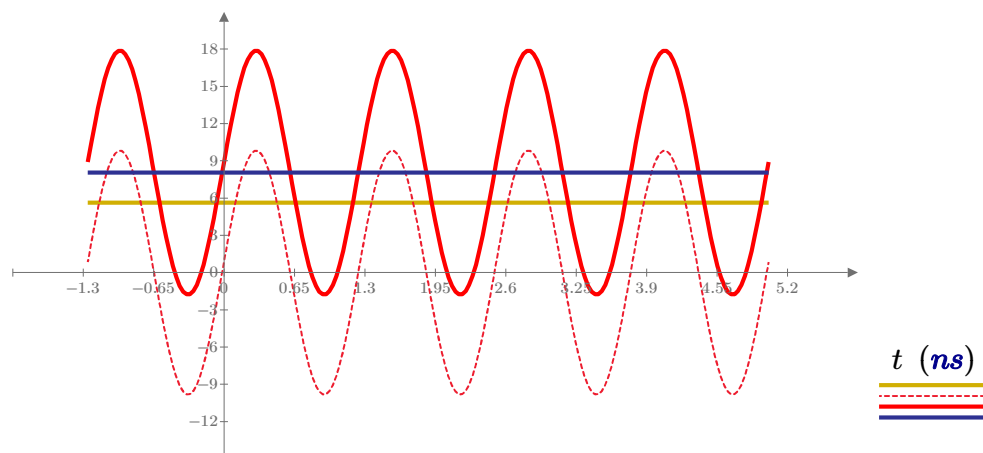

$$P_x := \begin{bmatrix} \text{Im}(P) \\ P \end{bmatrix} = \begin{bmatrix} 0 \\ 8.054 \end{bmatrix} \text{ mW}$$

$$P_y := \begin{bmatrix} \text{Im}(P) \\ \text{Im}(P) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \text{ mW}$$

$$Q_x := \begin{bmatrix} \text{Im}(P) \\ \text{Im}(P) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \text{ mW}$$

$$Q_y := \begin{bmatrix} \text{Im}(Q) \\ Q \end{bmatrix} = \begin{bmatrix} 0 \\ 5.638 \end{bmatrix} \text{ mW}$$


$$P_x + Q_x = \begin{bmatrix} 0 \\ 8.054 \end{bmatrix} \text{ mW}$$

$$P_y + Q_y = \begin{bmatrix} 0 \\ 5.638 \end{bmatrix} \text{ mW}$$

$$\frac{P_y \text{ (mW)}}{Q_y \text{ (mW)}}$$

$$\frac{Q_y \text{ (mW)}}{P_y + Q_y \text{ (mW)}}$$
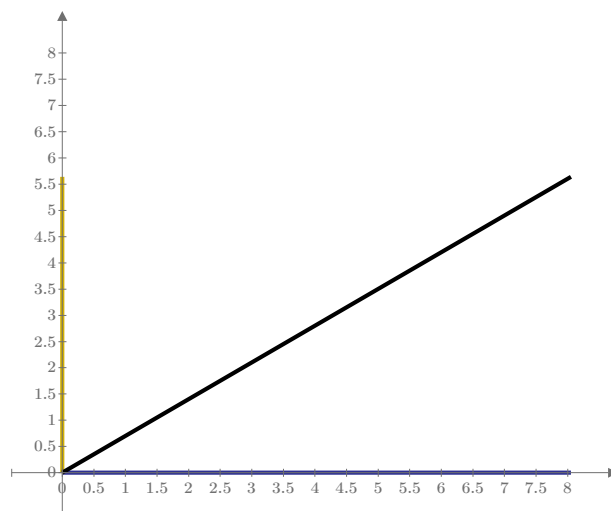
$$\frac{P_y + Q_y \text{ (mW)}}{P_x \text{ (mW)}}$$



$$\frac{P_x \text{ (mW)}}{Q_x \text{ (mW)}}$$

$$\frac{Q_x \text{ (mW)}}{P_x + Q_x \text{ (mW)}}$$

$$\frac{P_x + Q_x \text{ (mW)}}{P_x \text{ (mW)}}$$