

$$\omega = 2k \text{ rad/s}$$

$$v(t) = 5 \cdot \sin(2k \cdot t) \rightarrow \bar{V} = 5 \angle 22.5^\circ$$

1. Calcolare la corrente
2. Calcolare V_R , V_L e V_C
3. Verificare graficamente che $V = V_R + V_L + V_C$

1. Per il calcolare la corrente occorre prima calcolare l'impedenza totale:

$$\dot{Z}_{tot} = R + X_L + X_C = R + j\omega L + \frac{1}{j\omega C}$$

$$\begin{aligned} \dot{Z}_{tot} &= 200 + j2 \cdot 10^3 \cdot 50 \cdot 10^{-3} + \frac{1}{j2 \cdot 10^3 \cdot 1 \cdot 10^{-6}} \\ &= 200 + \underbrace{j100}_{X_L} - \underbrace{j500}_{X_C} = 200 - j400 \end{aligned}$$

Calcolo la Z_{tot} in notazione polare:

$$\dot{Z}_{tot} = \sqrt{200^2 + 400^2} \angle \arctan\left(\frac{-400}{200}\right) = 447.2 \angle -63.4^\circ$$

Ora posso calcolare la corrente:

$$\bar{I} = \frac{\bar{V}}{\dot{Z}_{tot}} = \frac{5 \angle 22.5^\circ}{447.2 \angle -63.4^\circ} = \frac{5}{447.2} \angle (22.5^\circ - (-63.4^\circ)) = 11.2 \text{mA} \angle 85.9^\circ$$


$$\text{Quindi: } i(t) = 11.2 \text{mA} \cdot \sin(2k \cdot t + 85.9^\circ)$$

2. Calcolo delle tensioni richieste

$$\begin{aligned} \bar{V}_R &= R \bar{I} = 200 \cdot (11.2 \text{mA} \angle 85.9^\circ) = \overbrace{2.24 \angle 85.9^\circ}^{\text{polare}} \\ &= 2.24 \cdot \cos(85.9^\circ) + j2.24 \cdot \sin(85.9^\circ) = \underbrace{0.159 + j 2.23}_{\text{cartesiana}} \end{aligned}$$


$$\begin{aligned} \bar{V}_L &= \dot{X}_L \bar{I} = j100 \cdot (11.2 \text{mA} \angle 85.9^\circ) = (100 \angle 90^\circ) \cdot (11.2 \text{mA} \angle 85.9^\circ) = \\ &= 100 \cdot 11.2 \text{mA} \angle (90^\circ + 85.9^\circ) = \overbrace{1.12 \angle 175.9^\circ}^{\text{polare}} \\ &= 1.12 \cdot \cos(175.9^\circ) + j1.12 \cdot \sin(175.9^\circ) = \underbrace{1.115 + j 0.079}_{\text{cartesiana}} \end{aligned}$$

$$\begin{aligned} \bar{V}_C &= \dot{X}_C \bar{I} = \frac{1}{j\omega C} \cdot (11.2 \text{mA} \angle 85.9^\circ) = -j500 \cdot (11.2 \text{mA} \angle 85.9^\circ) = (500 \angle -90^\circ) \cdot (11.2 \text{mA} \angle 85.9^\circ) = \\ &= 500 \cdot 11.2 \text{mA} \angle (-90^\circ + 85.9^\circ) = \overbrace{5.6 \angle -4.1^\circ}^{\text{polare}} \\ &= 5.6 \cdot \cos(-4.1^\circ) + j5.6 \cdot \sin(-4.1^\circ) = \underbrace{5.576 - j 0.396}_{\text{cartesiana}} \end{aligned}$$

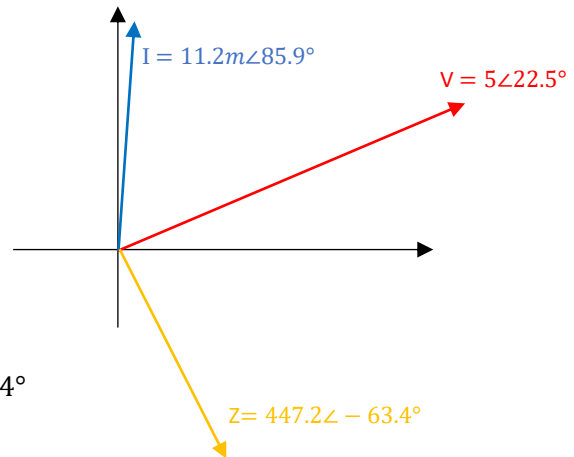

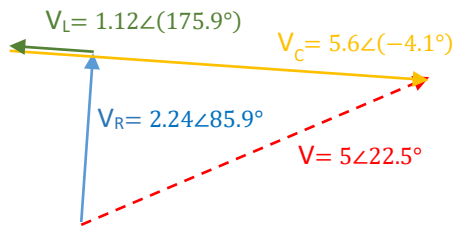3. Verifica grafica

Dalla figura sottostante è evidente che $V_R + V_L + V_C$ è uguale a V



Al medesimo risultato si poteva giungere per via matematica:

$$\bar{V} = 5 \angle 22.5^\circ = 5 \cdot \cos(22.5^\circ) + j5 \cdot \sin(22.5^\circ) = 4.619 + j1.913$$

$$\bar{V}_R + \bar{V}_L + \bar{V}_C = 0.159 + j2.23 + 1.115 + j0.079 + 5.576 - j0.396 = 4.619 + j1.913 = \bar{V}$$